

10 MAR 2021

[Total No. of Questions: 09]

[Total No. of Pages: 02]

Uni. Roll No.

Program/ Course: B.Tech. (Sem. 3rd)

Name of Subject: Network Analysis and Synthesis

Subject Code: PCEC-102

Paper ID: 16032

Time Allowed: 03 Hours

Max. Marks: 60

NOTE:

- 1) Parts A and B are compulsory
- 2) Part-C has Two Questions Q8 and Q9. Both are compulsory, but with internal choice
- 3) Any missing data may be assumed appropriately

Part – A

[Marks: 02 each]

Q1.

- a) State Superposition theorem.
- b) Differentiate dependent and independent sources.
- c) Find inverse Laplace transform of $F(s) = \frac{3s}{(s+2)(s+4)}$
- d) What is the significance of a 'pole' and a 'zero' in S- domain?
- e) Discuss the limitations of Const-K type filters
- f) Write the expression for Final Value theorem. Apply the same for the given function $\frac{(5s + 3)(s + 8)}{s(s + 1)(s + 2)}$

Part – B

[Marks: 04 each]

- Q2. A coil having resistance of 10 Ω and inductance of 1H is switched on to a direct voltage of 100V. Calculate the rate of change of the current (a) at the instant of closing the switch and (b) when $t=L/R$.
- Q3. State maximum power transfer theorem. Also, prove the condition; $R_L = R_{TH}$.
- Q4. Define "Impedance function". List the properties of R-C driving point impedance function.
- Q5. Design a Const-K type BPF to be terminated in 600 Ω resistance having cut-off frequencies of 2 KHz and 5 KHz.
- Q6. Explain in detail the concept of cut set and tie set.

Please check that this question paper contains 09 questions and 02 printed pages within first ten minutes.

EVENING
10 MAR 2021

Q7. State and prove Convolution theorem in pretext to network theory.

Part – C

[Marks: 12 each]

Q8. Define Thevenin's theorem. Write atleast its two limitations. Find the power loss in the 10Ω resistor in Figure 1.

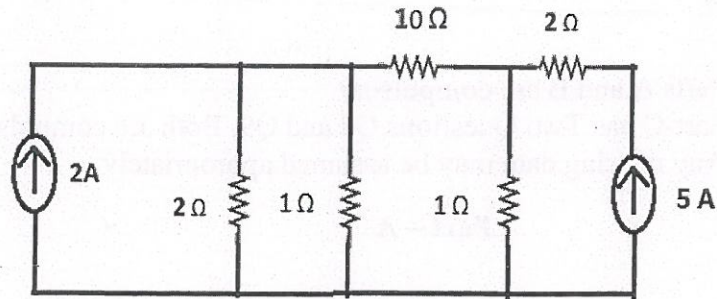


Figure 1

OR

Design the following networks for the impedance function

$$Z(s) = \frac{s(s^2 + 4)}{(s^2 + 1)(s^2 + 9)}$$

- (i) Foster-I
- (ii) Cauer-I

Q9. Prove that Norton's equivalent circuit is dual of Thevenin's equivalent circuit.

OR

State an advantage of m-derived filter over Cont-K type filter. Also, design an m-derived low pass filter to match a line having characteristic impedance of 500Ω and to pass signals upto 1 KHz with infinite attenuation occurring at 1.2 KHz.

PAGE 2 OF 2